

No. of Printed Pages : 03

Roll No.

CC-766

M. Tech. EXAMINATION, Dec. 2018

(Third Semester)

(B. Scheme) (Main & Re-appear)

(MTVLSI)

MTVLSI661

CMOS RF IC DESIGN

Time : 3 Hours]

[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all, selecting *one* question from each Unit. All questions carry equal marks.

(3-38/1) M-CC-766

P.T.O.

Unit I

1. Briefly describe the concept of noise, sensitivity, dynamic range and inter-symbol interference w.r.t. RF IC design. **15**
2. (a) Compare coherent and non-coherent detection techniques in RF IC design. **6**
(b) What do you understand by the terms modulation and detection in RF circuits ? Discuss in detail the operation of Digital modulation techniques of RF circuits. Also, give its various advantages, disadvantages and applications. **9**

Unit II

3. Discuss the following in detail : **8+7**
 - (a) MOSFET behaviour at RF frequencies
 - (b) Digital IF receiver and its applications Modeling of transistors.
4. Define the terms Heterodyne receiver and Two-step transmitter. Briefly explain the concept of Integrated parasitic elements at high frequencies in RF transistors. **15**

M-CC-766

2

Unit III

5. What is the role and significance of Mixer in RF circuits ? Discuss in detail the design of low noise amplifier. Also give its various applications. **15**
6. Describe the design and working of the following : **8+7**
 - (a) CMOS LC Oscillator
 - (b) Single sideband generator.

Unit IV

7. Explain the concept and general considerations of the following in detail : **8+7**
 - (a) Frequency dividers
 - (b) Noise in PLL.
8. Write short notes on the following : **8+7**
 - (a) RF power amplifier
 - (b) Linearization techniques and their advantages.

(3-38/2) M-CC-766

3

40