

No. of Printed Pages : 03

Roll No.

CC-766

M. Tech. EXAMINATION, May 2018

(Third Semester)

(Re-appear Only)

ECE(VLSI)

MTVLSI661

CMOS RF IC DESIGN

Time : 3 Hours]

[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

(3-28/19)M-CC-766

P.T.O.

Unit I

1. Briefly describe the following wrt RF Design : **8+7**
 - (a) Power efficiency, Noise and Dynamic range
 - (b) Random process, Non-linearity and Time variance.
2. (a) Compare Coherent and Non-coherent detection techniques. **7**
(b) What do you understand by the term Inter-symbol interference and conversion of gains in RF circuits ? Discuss in detail the working of Digital modulation. Also, give its various advantages, disadvantages and applications. **8**

Unit II

3. Discuss the following in detail : **7+8**
 - (a) Direct conversion transmitter
 - (b) Digital-IF receiver and Spice model.

M-CC-766

2

4. Define the terms Homodyne receiver and Image-reject receiver. Also, explain the concept of BJT behaviour at RF frequencies. **15**

Unit III

5. Define the terms VCO, Noise power and Mixer. Also, discuss in detail the Low noise amplifier design in RF circuits. **15**
6. Describe the working of the following : **8+7**
 - (a) CMOS LC Oscillator
 - (b) Quadrature signal and signal generators.

Unit IV

7. Explain the operation of the following in detail : **8+7**
 - (a) RF Synthesizer
 - (b) PLL.
8. Write short notes on the following : **8+7**
 - (a) High frequency power amplifier
 - (b) Linearization techniques.

(3-28/20)M-CC-766

3

??