

8. Enlist various general considerations of RF power amplifier. Also briefly describe classification of power amplifiers and importance of liberalization techniques.

15

No. of Printed Pages : 04

Roll No.

CC766

M.Tech. EXAMINATION, May 2019

(Third Semester)

(B. Scheme) (Re-appear)

ECE(VLSI)

MTVLSI661

CMOS RF IC DESIGN

Time : 3 Hours]

[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

M-CC766

4

60

(3-34/16)M-CC766

P.T.O.

Unit I

1. Briefly describe the role and importance of Power efficiency, Random process, distortion, Non-linearity and time variance w.r.t. RF IC design. **15**
2. (a) Compare analog and digital modulation of RF circuits. **7**
(b) What do you understand by the terms Inter-symbol interference and sensitivity in RF circuits ? Discuss in detail the operation of coherent of detection. Also, give its various advantages, disadvantages and applications. **8**

Unit II

3. Discuss the following w.r.t. RF transceiver and RF transistor :
 - (a) Two-step transmitter
 - (b) Modeling of transistor and Space model.**7+8**

M-CC766

2

4. Make a comparison between Homodyne receiver, Heterodyne receiver and Image-reject receiver. Also, explain the concept of BJT behaviour at RF frequencies. **15**

Unit III

5. Define the terms VCO, phase noise and Mixer. Also discuss the design of Mixers at GHz frequency range in RF circuits. Give its various applications. **15**
6. Describe the design and operation of the following :
 - (a) Bipolar LC Oscillator
 - (b) Quadrature signal generator.**8+7**

Unit IV

7. Explain the following :
 - (a) RF Synthesizer architecture
 - (b) Types of PLL and their applications.

8+7

(3-34/17)M-CC766

3

P.T.O.