

Unit III

6. (a) Realize NAND and NOR gate with the help of switch and lamp logic. **5**
- (b) Convert the following :
 $(248.CF3)_{16} = ()_2$
 $(348.28)_8 = ()_{10}$ **5**
- (c) Realize EX-OR gate with only four NAND gates. **5**
7. (a) Draw and explain the block diagram of multimeter. **7½**
- (b) Draw and explain the block diagram of CRO. **7½**

Unit IV

8. (a) Why do we require modulation ? Explain how AM takes place. **7½**
- (b) Compare FM and PM. **7½**

No. of Printed Pages : 05

Roll No.

B3

B.Tech. EXAMINATION, May 2019

(Second Semester)

(B. Scheme) (Re-appear Only)

ECE102B

BASICS OF ELECTRONICS ENGINEERING

(Common with all Branches)

Time : 3 Hours]

[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all. Q. No. **1** is compulsory. Attempt any *four* from remaining eight and at least *one* question from each Unit.

1. (a) Differentiate between extrinsic and intrinsic semiconductor on the basis of fermi level.
- (b) How does Hall's effect help in distinguishing between extrinsic P-type and N-type semiconductor ?
- (c) How two diodes connected back to back gives rise to a transistor ?
- (d) What are the parameters of a voltage regulators ?
- (e) Why do interrupt 5.5, 6.5 and 7.5 are given names in decimals ? **5×3=15**

Unit I

2. (a) If two diodes are connected back to back across a battery of 10 V and a resistance of $100\ \Omega$? Then find voltage across each diode if they are :
 - (i) Both are forward biased
 - (ii) Both are reverse biased
 - (iii) Connected back to back. **7½**

- (b) Explain the working of half wave rectifier. Derive expression for V_{dc} and V_{rms} . **7½**

3. (a) Draw and explain O/P characteristics of CB configuration. Explain what is early effect ? **7½**
- (b) What are current components in a transistor ? Explain by using C.B. (PNP) configuration. **7½**

Unit II

4. (a) Realize OP Amp in Inverting mode as Summer, Averager and Scaling Amplifier. **7½**
- (b) Draw and explain working of differential amplifier. **7½**
5. (a) Explain the working of SMPS with the help block diagram. **7½**
- (b) Draw and explain the working of voltage regulator. **7½**

9. Write short notes on the following :

- (a) Interrupt structure of 8085 7½
- (b) Instructions :
 - (i) LDAX
 - (ii) STA
 - (iii) XCHG

Complete the format and explain in detail.

7½

9. Write short notes on the following :

- (a) Interrupt structure of 8085 7½
- (b) Instructions :
 - (i) LDAX
 - (ii) STA
 - (iii) XCHG

Complete the format and explain in detail.

7½