

No. of Printed Pages : 04

Roll No. ....

**C22**

**B. Tech. EXAMINATION, 2020**

(Third Semester)

(B Scheme) (Re-appear Only)

(ECE)

EE211B

NETWORK ANALYSIS AND SYNTHESIS

*Time : 2½ Hours]*

*[Maximum Marks : 75*

---

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

---

**Note :** Attempt *Four* questions in all. All questions carry equal marks.

(5)M-C22

1

1. Find the Laplace transforms of the following functions :

(a)  $e^{-at} U(t)$

(b)  $e^{-at} U(t - b)$

(c)  $e^{-a(t-b)} U(t - b) = e^{ab} \cdot e^{-at} U(t - b)$

(d)  $e^{-a(t-b)} U(t - c) = e^{ab} \cdot e^{-at} U(t - c).$

2. Find the response of the system whose system function  $H(s) = Y(s)/X(s) = 1/s + 1$  for the input :

(i)  $x(t) = \delta(t)$  (i.e. impulse response)

(ii)  $x(t) = e^{-2t}.$

3. Show that the overall transmission parameter matrix for cascaded Two 2-port networks is simply the matrix products of transmission parameters for each individual 2-port network in cascade.

4. A two-port T-network has open circuit impedances  $Z_{10} = 900 \text{ ohm}$ ,  $Z_{20} = 900 \text{ ohm}$  and short circuit impedance  $Z_{1s} = 650 \text{ ohm}$ . Determine the parameters of the T-network.
5. (a) Design a low pass filter (both  $\pi(pi)$  and T-networks) having a cut-off frequency of 1 kHz to operate with a terminated load resistance of 200 ohms.
- (b) Find the frequency at which this filter offers attenuation of 19.1 dB.
6. The reduced incidence matrix of a graph is given by :

Nodes\Branches	1	2	3	4	5	6
$a$	0	1	0	-1	-1	1
$b$	0	-1	1	0	1	0
$c$	1	0	-1	0	0	0

Draw the oriented graph. Select a tree and find  $f$ -cut set matrix.

7. Test the following polynomial for its Hurwitz Character :

$$P(s) = s^8 + 3s^7 + 10s^6 + 24s^5 + 35s^4 \\ + 57s^3 + 50s^2 + 36s + 24.$$

8. An impedance is given by :

$$Z(s) = \frac{8(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s^2 + 4)}$$

Realize the network in (i) Foster-I form and  
(ii) Cauer-II form.