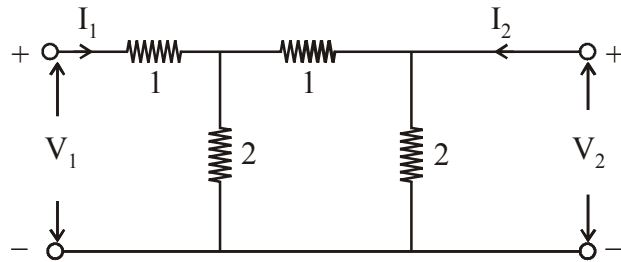


- (b) Explain significance of poles and zeros in network functions. 8

4. (a) Determine transmission parameters for networks in cascade. 7½
- (b) Determine Y-parameters in terms Z-parameters. 7½

### Unit III

5. Obtain ABCD parameters for the network shown in Fig. : 15



6. (a) What do you mean by prototype band pass filter ? Discuss its characteristics. 7½
- (b) How many trees are possible for the graph of network of given fig. ? 7½

No. of Printed Pages : 05

Roll No. ....

**C-22**

**B. Tech. EXAMINATION, Dec. 2017**

(Third Semester)

(B. Scheme) (Main & Re-appear)

(ECE, AEI)

EE-211-B

NETWORK ANALYSIS AND SYNTHESIS

Time : 3 Hours]


[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.


**Note :** Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

## Unit I

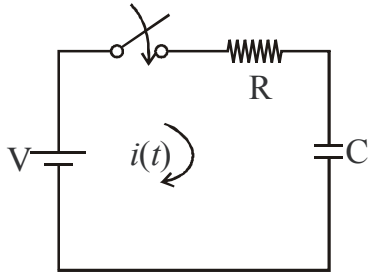1. (a) Derive an expression for transient response of RL circuit to a unit step input. 8
- (b) Derive an expression of voltage across resistor and capacitor in given circuit, when  $t > 0$ . 7



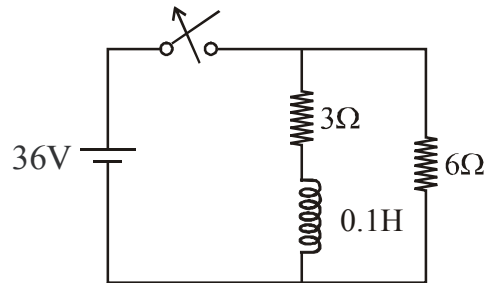
2. (a) In the network of under giving fig. the switch is opened at  $t = 0$ . Find  $i(t)$ . 8



M-C-22


2

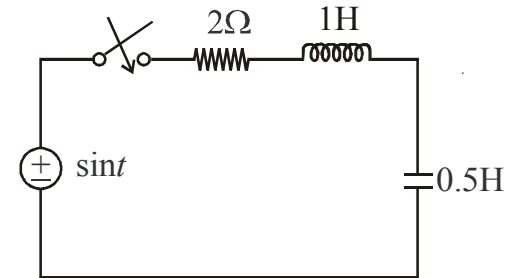- (b) For the network shown in under fig., the switch is closed at  $t = 0$ . Determine the current  $i(t)$  assuming zero initial conditions. 7



## Unit II

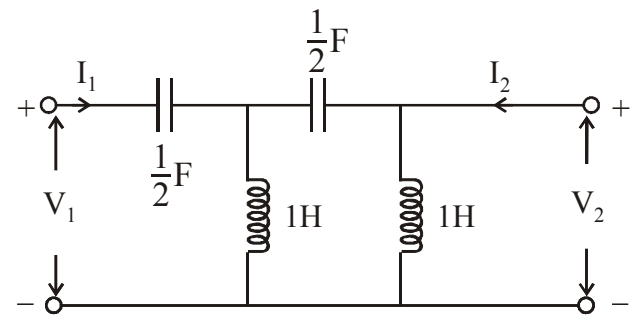
3. (a) Find  $h$ -parameters for networks shown in fig. : 7



(2-56/7) M-C-22

3

P.T.O.

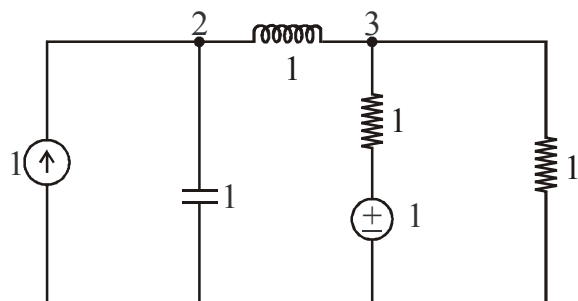

#### Unit IV


7. (a) Explain the properties of positive real functions. 7½
- (b) Test whether the polynomial  $P(s)$  is Hurwitz. 7½

$$P(s) = s^5 + s^3 + s$$

8. (a) Determine the foster form of realisation of the RC impedance function : 10

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$$

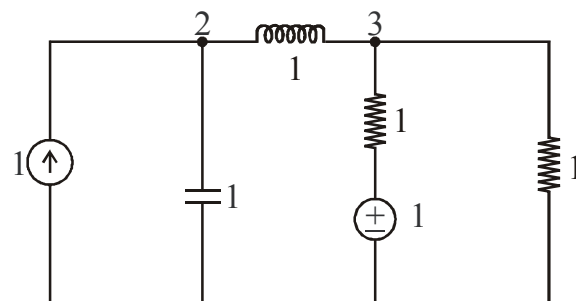- (b) Define tree, co-tree, tieset, cutset, incidence matrix. 5



#### Unit IV

7. (a) Explain the properties of positive real functions. 7½
- (b) Test whether the polynomial  $P(s)$  is Hurwitz. 7½

$$P(s) = s^5 + s^3 + s$$

8. (a) Determine the foster form of realisation of the RC impedance function : 10

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$$

- (b) Define tree, co-tree, tieset, cutset, incidence matrix. 5