

6. Explain, how do we find ABCD parameters in terms of Z-parameters and also discuss how do we find transmission parameters for reciprocal network. **15**

Unit IV

7. The transform voltage $V(s)$ of a network is given by :

$$V(s) = \frac{4s}{(s+2)(s^2+2s+2)}$$

Plot its pole-zero diagram and hence obtain $v(t)$. **15**

8. Realize the network function

$$Z(s) = \frac{s(s^2+4)}{2(s^2+1)(s^2+9)} \text{ in Cauer forms. } \mathbf{15}$$

No. of Printed Pages : 04

Roll No.

C-22

B. Tech. EXAMINATION, Dec. 2018

(Third Semester)

(B. Scheme) (Main & Re-appear)

(ECE)

EE211B

NETWORK ANALYSIS AND SYNTHESIS

Time : 3 Hours]

[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

Unit I

1. (a) Discuss transient response of RC circuit with step current response. **8**
(b) Discuss the application of Laplace transform of complex waveform. **7**
2. Explain and derive the complete response of R-L-C circuit to step current response. **15**

Unit II

3. Design m -derived T and π sections of a high pass filter having design impedance of 600 ohms, cut off frequency of 5 kHz and $m = 0.35$. Find also the frequency of infinite attenuation. **15**
4. Explain the following terms : **15**
 - (a) Linear Graph
 - (b) Branch
 - (c) Node
 - (d) Connected Graph

- (e) Unconnected Graph
- (f) Oriented Graph
- (g) Loop
- (h) Tree
- (i) Link
- (j) Cut-set
- (k) Incidence matrix
- (l) Cut-set matrix
- (m) Fundamental Loop
- (n) Fundamental Loop Matrix
- (o) Fundamental Cut-Sets.

Unit III

5. Find the transmission parameters for network given below in fig. (i) as : **15**

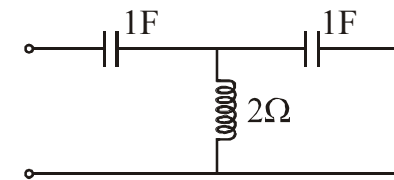


Fig (i)