

No. of Printed Pages : 03

Roll No. ....

**W-621**

**B. Tech. EXAMINATION, Dec. 2017**

(Sixth Semester)

(Weekend) (Re-appear Only)

(ECE)

ECE-W-302

**MOS IC'S AND TECHNOLOGY**

*Time : 3 Hours]*

*[Maximum Marks : 100*

---

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

---

**Note :** Attempt any *Five* questions. All questions carry equal marks.

1. Explain N-MOS and CMOS fabrication process with neat diagrams. **20**

(2-21/11) M-W-621

**P.T.O.**

2. (a) Give derivation for transconductance  $G_m$  for MOS transistor. **7**

(b) Find the drain current for an nMOS having :

$$\mu_n C_{ox} = 150 \mu A/V^2,$$

$$W = 1 \mu m$$

$$L = 0.25 \mu m$$

$$V_{GS} = 1.5 V$$

$$V_{tn} = 0.5 V$$

$$V_{DS} = 2.0 V$$

(c) Derive the CMOS Inverter DC characteristics, show all operating regions and explain it.

3. (a) What is photolithography ? Explain its various steps in detail. **10**

(b) Explain the epitaxial growth process in IC fabrication. How it is done ? Why is it needed ? **10**

4. Explain the following :

(a) Resistance Estimation

(b) Capacitance Estimation. **10**

5. Design the following function by using nMOS and CMOS logic. Explain why, NAND gate are preferred over NOR gate ? **20**

6. What do you mean by power dissipation in MOS ICs ? Out of NMOS and PMOS which one is having more power dissipation and why ? **20**

7. What do you mean by power dissipation in MOS ICs ? Out of NMOS and PMOS which one is having more power dissipation and why ? **20**

8. Explain a two-phase non-overlapping clock generator with buffered output on both phases with the help of suitable diagram. **20**