

No. of Printed Pages : 04

Roll No. ....

**C13**

**B. Tech. EXAMINATION, 2020**

(Third Semester)

(B Scheme) (Re-appear Only)

(EE, EEE)

EE203B

NETWORK ANALYSIS-I

*Time : 2½ Hours]*

*[Maximum Marks : 75*

---

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.


---

**Note :** Attempt *Four* questions in all. All questions carry equal marks.

(2)M-C13

1

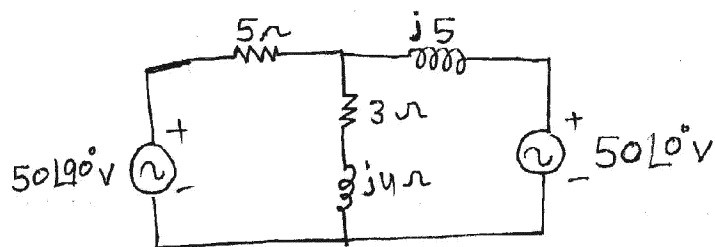
1. (a) A circuit consists of three parallel branches. The branch currents are given as  $i_1 = 10 \sin wt$ ;  $i_2 = 20 \sin (wt + 60)$  and  $i_3 = 7.5 \sin (wt - 30)$ . Find the resultant current and express it in the form  $i = I_m(wt + \phi)$ . If the supply frequency is 50 Hz, calculate the resultant current when (a)  $t = 0$ , (b)  $t = 0.001$ s.
- (b) State and explain maximum power transfer theorem with an example.
2. Find the current through the  $(3 + j4)$  ohm impedance in the network by superposition theorem and verify the result by Nodal analysis :




3. (a) A balanced star connected load is supplied by a 415V; 50 Hz three phase
- (2)M-C13 2

system. Current in each phase is 20 A and lags  $30^\circ$  behind its phase voltage find the (a) phase voltage (b) power (c) circuit parameters. Also power consumed when the same load is connected in delta across the same supply.

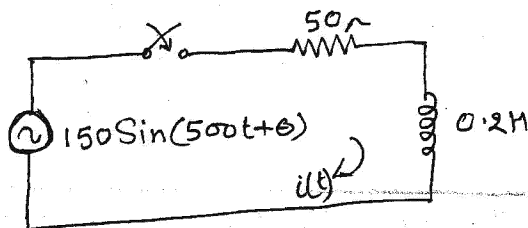
- (b) Explain p-spice model for poly-phase circuits.
4. (a) A certain wave form has a form factor of 1.2 and a peak factor of 1.5. If the maximum value is 100, find the RMS value and average value.
- (b) Derive an expression for line and phase voltages and currents relationship in case of delta connection.
5. For the network shown in fig. a sinusoidal voltage source  $v = 150 \sin(500t + \theta)$  volts is applied at a time when  $\theta = 0$ . Find the expression for the current  $i(t)$ .



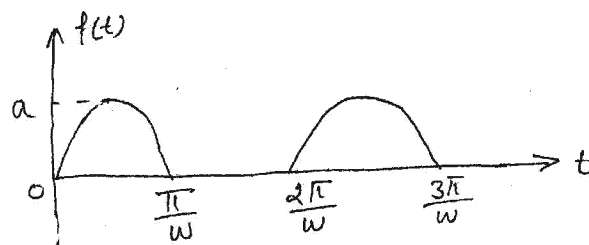6. Find Laplace transform of the waveform shown in Fig. :



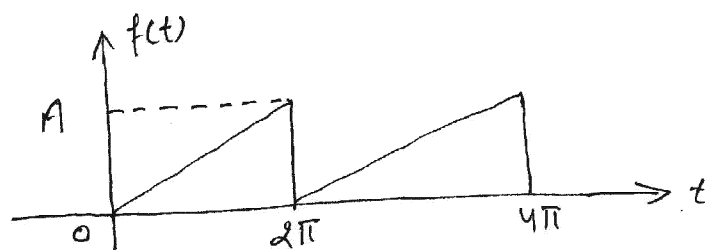7. Find trigonometric Fourier series of wave form shown in fig. draw the magnitude and phase spectrum :



8. Evaluate the Fourier series coefficient of the continuous time period signal :

$$x(t) : X(t) = 1 + \sin \omega t + 2 \cos \omega t + \cos [2\omega t + \pi/4]$$

(2)M-C13