

$\eta = 0.7$, $I_p = 0.5 \text{ mA}$, $V_p = 15.0 \text{ V}$, $V_u = 0.8 \text{ V}$,
 $I_u = 2 \text{ mA}$, $R_{BB} = 6 \text{ k}\Omega$.

Normal leakage current with emitter open = 3 mA. The firing frequency is 1.5 kHz for $C = 0.05 \text{ }\mu\text{F}$. Compute the values of charging resistor and the external resistors connected in the base circuits. Take forward-voltage drop of E-B, Junction as zero and if the frequency of firing of SCR in above problem is changed by varying charging resistor R , obtain the maximum and minimum values of R and corresponding frequencies. **15**

8. (a) Differentiate natural and forced commutation. **7½**
- (b) With the help of suitable diagrams, explain Class D and Class E commutation. **7½**

No. of Printed Pages : 04

Roll No.

C-15

B. Tech. EXAMINATION, Dec. 2018

(Third Semester)

(B. Scheme) (Main & Re-appear)

(EE, EEE)

EE207B

POWER ELECTRONICS DEVICES

Time : 3 Hours]

[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

Unit I

1. (a) Describe the construction and working of LED. 7½
(b) A single-phase half wave uncontrolled rectifier is connected to RL load. Derive an expression for the load current in terms of v_m , z , w . 7½
2. (a) Explain saturation and cut-off mode of operation of BJT. 7½
(b) Describe Eber-moll's model in detail. 7½

Unit II

3. (a) Explain following terms in detail for Biasing : 7½
(i) Collector to base Bias
(ii) Self-bias
(iii) Emitter Bias.
(b) Describe construction and characteristics of power transistors. 7½

M-C-15

2

4. (a) Discuss applications of FET as a VVR. 7½
(b) Explain construction and working of Power MOSFET. 7½

Unit III

5. (a) Explain the role and applications of power electronics in recent time. 7½
(b) Describe BENISTOR in detail. 7½
6. Explain the following in detail : 15
(a) GTO
(b) DIAC
(c) TRIAC
(d) Metal oxide controlled thyristor.

Unit IV

7. A Relaxation oscillator, using an UJT, is to be designed for Triggering an SCR the UJT has the following data :

(3-13/12)M-C-15

3

P.T.O.