

### Unit III

No. of Printed Pages : 05

Roll No. ....

5. Give an algorithm to solve load flow equations using decoupled load flow. Consider both PQ and PV buses. **15**

6. The following is the system data for a load flow solution :

The line admittances :

Impedance for sample system :

Bus Code	Admittance
1-2	$2-j8.0$
1-3	$1-j4.0$
2-3	$0.666+j2.664$
2-4	$1-j4.0$
3-4	$2-j8.0$

The schedule of active and reactive powers are :

Bus Code	P	Q	V	Remarks
1	—	—	1.06	Slack
2	0.5	0.2	$1+j0.0$	PQ
3	0.4	0.3	$1+j0.0$	PQ
4	0.3	0.1	$1+j0.0$	PQ

Determine the voltages at the end of first iteration by using Gauss-Siedel method. Take  $\alpha = 1.6$ . **15**

## H-22

### B. Tech. EXAMINATION, Dec. 2017

(Eighth Semester)

(B. Scheme) (Re-appear Only)

(EE, EEE)

EE-404-B

### COMPUTER APPLICATIONS TO POWER SYSTEM ANALYSIS

Time : 3 Hours]

[Maximum Marks : 75

---

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

---

**Note :** Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

## Unit I

1. Describe in detail the power flow equations of transmission lines. **15**
2. (a) Define and explain the following : **6**
  - (i) tree
  - (ii) co-tree
  - (iii) link
  - (iv) graph with the help of examples.
- (b) Find fundamental cut-set matrix and obtain KCL equations of fig. (1). **9**

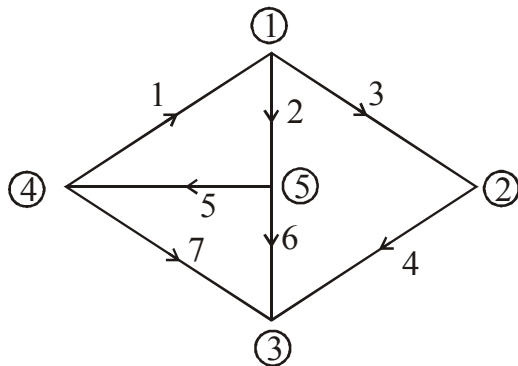


Fig. 1

## Unit II

3. (a) Describe the terms primitive admittance matrix and incidence matrix. **6**
- (b) Describe in detail the steps involved in the building algorithm for the bus impedance matrix. **9**
4. (a) Develop an expression for  $Z_{\text{Bus}}$  (Bus impedance matrix) using bus incidence matrix A formulation. **7**
- (b) A primitive Y matrix is :

$$\begin{matrix}
 & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\
 \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} & \begin{pmatrix} 2.083 & -0.417 & 0 & -1.042 & 0 \\ -0.417 & 2.083 & 0 & 0.208 & 0 \\ 0 & 0 & 2.0 & 0 & 0 \\ -1.042 & 0.208 & 0 & 3.021 & 0 \\ 0 & 0 & 0 & 0 & 5 \end{pmatrix}
 \end{matrix}$$

Form  $Y_{\text{Bus}}$ .

**8**

#### Unit IV

7. (a) Derive an expression for fault current for single line-to-ground fault. 7
- (b) A 3-phase, 11 kV, 25 MVA generator with  $X_0 = 0.05$  p.u.,  $X_1 = 0.2$  p.u. and  $X_2 = 0.2$  p.u. is grounded through a reactance of 0.3. Calculate the fault currents for a single line to ground fault. 8
8. (a) Express unbalanced phase currents in a 3- $\phi$  system in terms of symmetrical components. 7
- (b) The voltages across a 3- $\phi$  unbalanced load are  $V_a = 300$  V,  $V_b = 300\angle -90^\circ$  and  $V_c = 800\angle 143.1^\circ$  respectively. Determine the sequence components of voltages. Phase sequence is *abc*. 8

#### Unit IV

7. (a) Derive an expression for fault current for single line-to-ground fault. 7
- (b) A 3-phase, 11 kV, 25 MVA generator with  $X_0 = 0.05$  p.u.,  $X_1 = 0.2$  p.u. and  $X_2 = 0.2$  p.u. is grounded through a reactance of 0.3. Calculate the fault currents for a single line to ground fault. 8
8. (a) Express unbalanced phase currents in a 3- $\phi$  system in terms of symmetrical components. 7
- (b) The voltages across a 3- $\phi$  unbalanced load are  $V_a = 300$  V,  $V_b = 300\angle -90^\circ$  and  $V_c = 800\angle 143.1^\circ$  respectively. Determine the sequence components of voltages. Phase sequence is *abc*. 8