

No. of Printed Pages : 03

Roll No. ....

**E13**

**B. Tech. EXAMINATION, 2020**

(Fifth Semester)

(B-Scheme) (Re-appear Only)

EE, EEE & IC

ECE311B

INTEGRATED ELECTRONICS

*Time : 2½ Hours]*

*[Maximum Marks : 75*

---

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

---

**Note :** Attempt *Four* questions in all. All questions carry equal marks.

1. (a) Explain distortions in amplifiers.  
(b) What is the effect of emitter bypass capacitor on low frequency response of an amplifier ?
2. Give analysis of transistor amplifier circuit using hybrid parameters at low frequencies.
3. Draw and explain different types of feedback topologies.
4. (a) Explain RC phase shift oscillator with proper illustrations and mathematical expressions.  
(b) Explain Barkhausen criterion.
5. (a) Explain and Draw Circuit diagram of push pull amplifiers.  
(b) What is harmonic distortion ?
6. (a) List six characteristics of ideal OPAMP.  
(b) Define CMRR, Common mode signal, Difference mode signal and offset voltages.

7. (a) Draw circuit and explain voltage to current converter.  
(b) Explain Integrator with circuit diagram and mathematical expression.
8. (a) Explain Sample and hold circuit.  
(b) Explain Logarithmic amplifier with circuit diagram and mathematical expression.