

- (b) Write short notes on the following semiconductor memories :

- (i) SRAM
- (ii) DRAM
- (iii) PROM
- (iv) EPROM. 8

### Unit III

6. (a) Discuss the construction and working of Parallel in-Parallel out Shift registers. 8
- (b) Draw the block diagram of a 3-bit asynchronous counter and explain its operation. 7
7. (a) Explain the operation and timing diagram of outputs of a synchronous counter. 9
- (b) Discuss the important applications of Shift Registers. 6

M-18BB1802

4

No. of Printed Pages : 05

Roll No. ....

**18BB1802**

**M. Sc. EXAMINATION, May 2019**

(Second Semester)

(C Scheme) (Main Only)

PHYSICS

PHY504C

Electronics-II

*Time : 3 Hours]*

*[Maximum Marks : 75*

---

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

---

**Note :** Q. No. 1 is compulsory. Attempt *Five* questions in all including the compulsory question and select at least *one* question from each Unit. All questions carry equal marks.

(3-42/3) M-18BB1802

P.T.O.

1. (a) How the full adder is beneficial over half adder ?
- (b) Explain accuracy and resolution of a DAC.
- (c) Differentiate between decoder and demultiplexer.
- (d) What is meant by up/down counter ?
- (e) Why are registers required in microprocessor ? 3×5=15

### Unit I

2. (a) Discuss the circuit diagram and operation of CMOS NAND gate. 6
- (b) Use a Karnaugh map to reduce the given expression to a minimum SOP form :  

$$\bar{A}BC + A\bar{B}\bar{C} + ABC + AB\bar{C}$$
 5
- (c) Explain the operation of a Decimal to BCD Encoder. 4

M-18BB1802

2

3. (a) Discuss the circuit diagram, operation and characteristics of DTL Circuit. 7
- (b) Write short notes on the following :
  - (i) J-K flip-flop
  - (ii) Multiplexer
  - (iii) ECL
  - (iv) TTL. 8

### Unit II

4. (a) Explain CAM and other advanced memories. 7
- (b) Discuss digital ramp analog to digital converter with necessary circuit diagram. 8
5. (a) Discuss digital to analog conversion technique using resistor ladder network. 7

(3-42/4) M-18BB1802

3

P.T.O.

#### **Unit IV**

8. Describe the pin diagram of 8085 microprocessor. Discuss the working of each unit used in it. **15**
9. (a) Explain internal architecture and working of 8085 microprocessor. **10**
- (b) What is the difference between microprocessor and microcontroller ? **5**

#### **Unit IV**

8. Describe the pin diagram of 8085 microprocessor. Discuss the working of each unit used in it. **15**
9. (a) Explain internal architecture and working of 8085 microprocessor. **10**
- (b) What is the difference between microprocessor and microcontroller ? **5**