

6. (a) What are various design constraints of a CMOS comparator ? **5**
- (b) What are various methods of compensating 2 stage Op-Amp. **10**

Unit IV

7. (a) Implement a simple PLL in CMOS technology. **5**
- (b) Write short notes on the following : **10**
- (i) PLL as frequency multiplier
- (ii) OTA.
8. What are various types of CMOS ADC ? Model a generalized ADC in CMOS technology. **15**

No. of Printed Pages : 04

Roll No.

BB-64

M. Tech. EXAMINATION, Dec. 2017

(Second Semester)

(B. Scheme) (Re-appear Only)

ECE/Industry Integrated

MTEC-508-B

ANALOG VLSI DESIGN

Time : 3 Hours]

[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.


Unit I

1. (a) Explain graphically, the variation of Gate-Source and Gate-Drain capacitance with Gate-Source Voltage. 7
(b) Discuss SPICE level-3 Model for CMOS. 8
2. (a) Model MOSFET as Diode. 9
(b) Draw MOS schematic of cascode current sink. 6

Unit II

3. (a) Derive transconductance of source follower. 7
(b) What are advantages of differential amplifier ? Draw its small signal equivalent. 8

 4. (a) Calculate small signal voltage gain of the following circuit : 5



- (b) What are application areas of Wilson current mirror ? Draw and explain its small signal equivalent. 10

Unit III

5. (a) Design a cascode Op-Amp for maximum differential swing of 2.4 V, total power dissipation of 6 mW. 10
(b) Explain concept of Gain Boosting in Op-Amp. 5